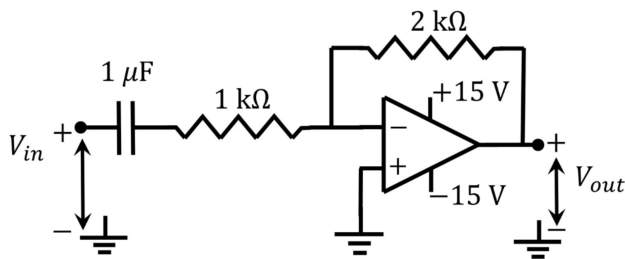


# Assignment

EE23BTECH11001 - Aashna Sahu

Q: An ideal OPAMP circuit with a sinusoidal input is shown in the figure. The 3dB frequency is the frequency at which the magnitude of the voltage gain decreases by 3 dB from the maximum value. Which of the options is/are correct?




- (A) The circuit is a low pass filter.
- (B) The circuit is a high pass filter.
- (C) The 3 dB frequency is 1000rad/s.
- (D) The 3 dB frequency is  $\frac{1000}{3}$  rad/s.

(GATE EC 2022)

**Solution:**

Parameter	Description	Value
$V_{in}$	Input Voltage	—
$V_{out}$	Output Voltage	—
$C$	Capacitor	$1\mu F$
$R_1$	Resistance	$1k\Omega$
$R_2$	Feedback Resistance	$2k\Omega$

TABLE 4: Input Parameters

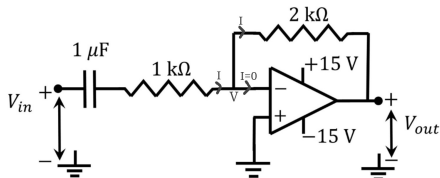

$$\frac{V_{in} - V}{\frac{1}{sC} + R_1} = \frac{V - V_{out}}{R_2} \quad (1)$$

As Op-Amp is ideal

$$V = V^+ = 0V \quad (2)$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{sCR_2}{1 + sCR_1} \quad (3)$$

$$H(s) = \frac{sCR_2}{1 + sCR_1} \quad (4)$$

For determining nature of Filter  
Put  $s = 0$

$$H(s) = 0 \quad (5)$$

Put  $s \rightarrow \infty$

$$H(s) = \frac{R_2}{R_1} = 2 \quad (\text{Finite}) \quad (6)$$

$\therefore$  It is high pass filter.

On simplifying (4) further

$$H(s) = \frac{R_2}{R_1} \left( \frac{s}{s + \frac{1}{CR_1}} \right) \quad (7)$$

$$|H(s)|_{max} = \frac{R_2}{R_1} \quad (8)$$

$$|H(s)|_{\omega=\omega_c} = \frac{R_2}{R_1} \left| \frac{s}{s + \frac{1}{CR_1}} \right| \quad (9)$$

Given

$$20 \log(|H(s)|_{max}) - 20 \log(|H(s)|_{\omega=\omega_c}) = 3dB \quad (10)$$

$$\frac{|H(s)|_{max}}{|H(s)|_{\omega=\omega_c}} = \sqrt{2} \quad (11)$$

From (8) and (9)

$$\frac{1}{\sqrt{2}} \frac{R_2}{R_1} = \frac{R_2}{R_1} \left| \frac{s}{s + \frac{1}{CR_1}} \right| \quad (12)$$

Put  $s = j\omega_c$

$$\left| \frac{j\omega_c}{j\omega_c + \frac{1}{CR_1}} \right| = \frac{1}{\sqrt{2}} \quad (13)$$

$$\Rightarrow \omega_c = \frac{1}{CR_1} \quad (14)$$

From Table 4

$$\omega_c = 1000 \text{ rad/s} \quad (15)$$

Where  $\omega_c$  is 3 dB frequency.

Finally, Correct options are (B) and (C).